

BLG222E Computer Organization

Project 2

Due Date: 07 JUNE 2021, 08:30

Design a **hardwired control unit** for the following architecture. Use the structure that you have designed in **Part 4 of Project 1**.

INSTRUCTION FORMAT

The instructions are stored in memory in **little endian order**. Since the RAM in Project 1 has 8-bit output, **IR** cannot be filled in one clock cycle. Fortunately, you have **L/H** signal in the **IR** and you can load MSB and LSB separately in two clock cycles:

- In the first clock cycle, **LSB** of the instruction must be loaded from an address **A** of the memory to **LSB of IR** [i.e., **IR(7-0)**].
- In the second clock cycle, **MSB** of the instruction must be loaded from an address **A+1** of the memory to **MSB of IR** [i.e., **IR(15-8)**].

There are two types of instructions as described below.

(1) Instructions with address reference have the format shown in Figure 1:

- The **OPCODE** is a **4-bit** field (See Table 1 for the definition).
- The next bit [i.e., **IR(11)**] is unused, you set it as 0
- The **ADDRESSING MODE** is a **1-bit** field (See Table 3 for the definition).
- The **REGSEL** is a **2-bit** field (See left side of Table 2 for the definition).
- The **ADDRESS** is an **8-bit** field.

OPCODE (4-bit)	0 (1-bit)	ADDRESSING MODE (1-bit)	REGSEL (2-bit)	ADDRESS (8-bit)
----------------	-----------	-------------------------	----------------	-----------------

Figure 1: Instructions with an address reference

(2) Instructions without address reference have the format shown in Figure 2:

- The **OPCODE** is a **4-bit** field (See Table 1 for the definition).
- The **DESTREG** is a **4-bit** field which specifies the destination register (See right side of Table 2 for the definition).
- The **SRCREG1** is a **4-bit** field which specifies the first source register (See right side of Table 2 for the definition).
- The **SRCREG2** is a **4-bit** field which specifies the second source register (See right side of Table 2 for the definition).

OPCODE (4-bit)	DESTREG (4-bit)	SRCREG1 (4-bit)	SRCREG2 (4-bit)
----------------	-----------------	-----------------	-----------------

Figure 2: Instructions without an address reference

Table 1: OPCODE field and SYMBOLs for operations and their descriptions

OPCODE (HEX)	SYMB	ADDRESSING MODE	DESCRIPTION
0x00	BRA	IM	PC \leftarrow Value
0x01	LD	IM, D	Rx \leftarrow Value (Value is described in Table 3)
0x02	ST	D	Value \leftarrow Rx
0x03	MOV	N/A	DESTREG \leftarrow SRCREG1
0x04	AND	N/A	DESTREG \leftarrow SRCREG1 AND SRCREG2
0x05	OR	N/A	DESTREG \leftarrow SRCREG1 OR SRCREG2
0x06	NOT	N/A	DESTREG \leftarrow NOT SRCREG1
0x07	ADD	N/A	DESTREG \leftarrow SRCREG1 + SRCREG2
0x08	SUB	N/A	DESTREG \leftarrow SRCREG2 - SRCREG1
0x09	LSR	N/A	DESTREG \leftarrow LSL SRCREG1
0x0A	LSL	N/A	DESTREG \leftarrow LSR SRCREG1
0x0B	PUL	N/A	M[SP] \leftarrow Rx, SP \leftarrow SP - 1
0x0C	PSH	N/A	SP \leftarrow SP + 1, Rx \leftarrow M[SP]
0x0D	INC	N/A	DESTREG \leftarrow SRCREG1 + 1
0x0E	DEC	N/A	DESTREG \leftarrow SRCREG1 - 1
0x0F	BNE	IM	IF Z=0 THEN PC \leftarrow Value

1101
1110

Table 2: REGSEL (Left) and DESTREG/SRCREG1/SRCREG2 (Right) select the register of interest for a particular instruction

REGSEL	REGISTER	DESTREG/SRCREG1/SRCREG2	REGISTER
00	R1	0000	PC
01	R2	0001	PC
10	R3	0010	AR
11	R4	0011	SP
		0100	R1
		0101	R2
		0110	R3
		0111	R4

Table 3: Addressing modes

ADDRESSING MODE	MODE	SYMB	Value
0	Direct	D	M[AR]
1	Immediate	IM	ADDRESS Field

EXAMPLE

Since PC value is initially 0, your code first executes the instruction in memory address 0x00. This instruction is **BRA START_ADDRESS** where **START_ADDRESS** is the starting address of your instructions.

The code given below adds data that are stored at memory addresses 0xA0, 0xA1, 0xA2, 0xA3, and 0xA4 (i.e., calculates **total** = $M[A0] + M[A1] + M[A2] + M[A3] + M[A4]$). Then, it stores the **total** in memory address 0xA6 (i.e., $M[A6]$). It is written as a loop that iterates 5 times.

You have to determine the binary code of the program and write it to the memory. Your final logisim implementation is expected to fetch the instructions starting from address 0x00, decode them and execute all instructions, one by one.

BRA 0x20	# This instruction is written to the memory address 0x00, # The first instruction must be written to the address 0x20
LD R1 IM 0x05	# This first instruction is written to the address 0x20, # R1 is used for iteration number
LD R2 IM 0x00	# R2 is used to store total
LD R3 IM 0xA0	
MOV AR R3	# AR is used to track data address: starts from 0xA0
LABEL: LD R3 D	# $R3 \leftarrow M[AR]$ (AR = 0xA0 to 0xA4)
ADD R2 R2 R3	# $R2 \leftarrow R2 + R3$ (Total = Total + $M[AR]$)
INC AR AR	# $AR \leftarrow AR + 1$ (Next Data)
DEC R1 R1	# $R1 \leftarrow R1 - 1$ (Decrement Iteration Counter)
BNE IM LABEL	# Go back to LABEL if Z=0 (Iteration Counter > 0)
INC AR AR	# $AR \leftarrow AR + 1$ (Total will be written to 0xA6)
ST R2 D	# $M[AR] \leftarrow R2$ (Store Total at 0xA6)

Submission:

Implement your design in logisim software, upload a single compressed (zip) file to Ninova before the deadline. **All the students from each group should submit the project file. Therefore, be sure that all of you uploaded the same final file to Ninova.** This compressed file should contain your design files (.circ) and a report that includes:

- the number&names of the students in the group
- information about your control unit design

Group work is expected for this project. All the 3 student members of the group **must** design together. Make sure to connect pins (under Wiring group of logisim) to the inputs and control inputs of your design, so that different inputs and functions can be tested. Similarly connect your inputs and outputs to a "Hex Digit Display" in logisim (under Input/output group of logisim) so that the test outputs can be observed and use proper labelling to improve the clarity of your circuits.